

item1 udonpittayanukoon

satha_por_n@Hotmail.com

Let $I = -I_0 \cos(\theta)$

question1 $V_L = ?$

ans1 $V_L = L di/dt$

$$V_L = [-L I_0] d \cos(\theta) / dt$$

$$V_L = [-L I_0] [-\sin(\theta)] [d(\theta) / dt]$$

$$V_L = [-L I_0] [-\sin(\theta)] [\omega]$$

$$V_L = [+ \omega L] [I_0] [\sin(\theta)]$$

$$V_L = [X_L] [I_0] [\sin(\theta)]$$

$$V_L = V_0 \sin(\theta)$$

question2 $V_R = ?$

ans2 $V_R = I \cdot R$

$$V_R = [-I_0 \cos(\theta)] \cdot R$$

$$V_R = [-I_0 \cdot R] \cos(\theta)$$

$$V_R = -V_{R_0} \cos(\theta)$$

question3 $V_C = ?$

ans3 Let ; $V_C = V_0 \sin(\theta + \text{phase})$

$$Q = C \cdot V$$

$$i_C = dQ/dt = -I_0 \cos(\theta)$$

$$d[+\sin(\theta)]/d(\theta) = +\cos(\theta)$$

$$d[-\sin(\theta)]/d(\theta) = -\cos(\theta)$$

$$i_C = [C] [-V_0 \sin(\theta) / dt] = -I_0 \cos(\theta)$$

$$[\omega C] [-V_0] \cos(\theta) = -I_0 \cos(\theta)$$

$$\omega C \cdot V_0 = I_0$$


$$V_0 / X_C = I_0$$

$$X_C = 1 / (\omega C) = 1 / (2\pi f C)$$

Then $V_C = -V_0 \sin(\theta)$

	input ; $i_0 =$	input; V_{L_0}	input $V_{R_0} =$
input	1	1	2
theta(deg.)	$i = -I_0 \cos(\theta)$	$V_L = V_{L_0} \sin(\theta)$	$V_R = -V_{R_0} \cos(\theta)$
0.00	-1.00	0.00	-2.00

45.00	-0.71	0.71	-1.41
90.00	0.00	1.00	0.00
135.00	0.71	0.71	1.41
180.00	1.00	0.00	2.00
225.00	0.71	-0.71	1.41
270.00	0.00	-1.00	0.00
315.00	-0.71	-0.71	-1.41
360.00	-1.00	0.00	-2.00
x-axis	y1	y2	y3

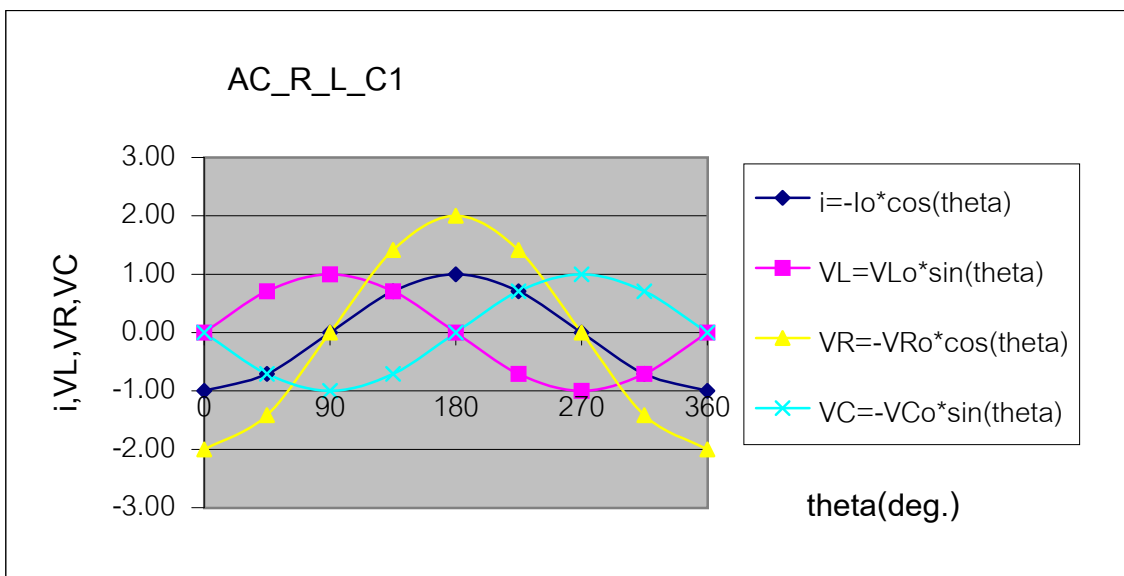

item2 RL_serires

question	L(henry)=?= Let1		$X_L = 2 * \pi() * f * L$ $I = I_m ** \sin(2 * \pi * f * t)$
no	var.	value	Excel_Code
1	f(Hz)=1000/(2*pi())	159.15	=1000/(2*PI())
2	$I_{max}(A)=$	5.00	=5
3	$V_{L,rms}(V)=$	70.70	=70.7
4	$V_L m = V_{rms} * \sqrt{2}$	99.98	= $\$C\$66 * \text{SQRT}(2)$

5	$X_L(\text{Ohm})=V_{Lm}/I_m$	20.00	= $\$C\$68/\$C\65
6	$L(\text{Henry})=X_L/(2*\pi*f)$	0.02	= $\$C\$69/(2*\pi()*\$C\$64)$

item3	RC_series		Note
Let1	$V_R(V)=0.15*\sin(500*t)$		$V_R(V)=0.15*\sin(2*\pi()*f*t)$
question	$V_{C,max}=?$		$V_{C,max}=I_{max}*X_C$
no.	var.	val	excel_code
1	$R(\text{Ohm})=$	30	=30
2	$C(\mu F)=$	2	=2
3	$V_R(V),max=$	0.15	=0.15
4	$f(\text{Hz.})=500/(2*\pi)$	79.57747155	= $500/(2*\pi())$
6	$X_C(\text{ohm})=1/(2*\pi()*f*C)$	1000	= $1/(2*\pi()*\$C\$81*\$C\$79*1E-6)$
7	$I_{max}(A)=V_{R,max}/R$	0.005	= $\$C\$80/\$C\78
8	$V_{C,max}(V)=I_{max}*X_C$	5	= $\$C\$83*\$C\82

item4	RLC_series		
Question1	$C=?$		
condition1	$IF X_L=X_C$	resonance frequency	
condition2	$2*\pi()*f*L=1/[2*\pi()*f*C]$		
condition3	$f_{res.}=1/[2\pi*\sqrt{L*C}]$		
condition4	$\omega^2=1/(L*C)$		
no.	var.	value	Excel_code
1	angular speed, $\omega(\text{rad/s})=2\pi f$	1.00E+07	=1e+7
2	$L(H)=$	1.00E-04	=100e-6
3	$C(\text{F, farad})=1/[L*\omega.2]$	1.00E-10	= $1/(\$C\$96*\$C\$95^2)$
4	$C(\text{pF})=$	1.00E+02	= $\$C\$97*1e+12$

item5 RLC_series

question	$V_{RLC,rms}(V)=I_{rms} \cdot Z_{RLC}$		Ohm's law
no.	var.	value	Excel_code
1	$R(OHM)=$	12	=12
2	$X_L(OHM)=$	36	=36
3	$X_C(OHM)=$	20	=20
4	$V_{R,rms}(V)=$	6	=6
7	$Z_{RLC}^2=R^2+(X_L-X_C)^2$	400	= $\$C\$107^2+(\$C\$108-\$C\$109)^2$
8	$Z_{RLC}=\text{sqrt}(R^2+(X_L-X_C)^2)$	20	=SQRT($\$C\111)
9	$I_{rms}=V_{R,rms}/R$	0.5	= $\$C\$110/\$C\107
10	$V_{RLC,rms}(V)=I_{rms} \cdot Z_{RLC}$	10	= $\$C\$113 \cdot \$C\112

item6	(RLC_series)//V5V.AC	$X_C(Ohm)=?$	Question
	$V_{RLC}^2=V_R^2+(V_L-V_C)^2$	Phase_vector_Addition	
no.	var	value	Excel_code
1	$V_{R,rms}(V)=$	4	=4
2	$V_{L,rms}(V)=$	6	=6
3	$R(Ohm)=$	8	=8
4	$V_{RLC}(V)$	5	=5
5	$V_C=V_L-\text{sqrt}(V_{RLC}^2-V_R^2)$	3	= $\$C\$121-\text{SQRT}(\$C\$123^2-\$C\$120^2)$
6	$I_{rms}(A)=V_{rms,R}/R$	0.5	=D120/ $\$C\122
7	$X_C(ohm)=V_{C,rms}/I_{rms}$	6	= $\$C\$124/\$C\125
8	$X_C(kohm)=$	0.006	=D126/1000

item7 power factor= $\cos\phi$

no $P_{\text{effective}}=I_{rms} \cdot V_{rms} \cdot \cos\phi$

1 power factor= $\cos\phi=R/Z$

2 $Z=\text{sqrt}(R^2+(X_L-X_C)^2)$ RLC_series

3 IF $X_L=X_C$ resonace frequency

4 $Z=\text{sqrt}(R^2+(0)^2)$ resonace frequency


5 $Z=R$ resonance frequency

6 $\cos\phi=R/Z=R/R=1$ resonance frequency


7 $1/Z=\sqrt{[(1/R)^2+(1/X_C-1/X_L)^2]}$ RLC_parallele

8 $1/Z=\sqrt{[(1/R)^2+(1/X_C-1/X_L)^2]}$


			L(mH)
			10
no._RLC_s	f(Hz)	R(Ohm)	$X_L(\text{Ohm})=2*\pi()*f*L$
1	50	10	3.14
2	100	10	6.28
3	150	10	9.42
4	200	10	12.57
5	250	10	15.71
6	300	10	18.85
7	350	10	21.99
8	400	10	25.13
9	450	10	28.27
10	500	10	31.42
	X-axis	y1	y2

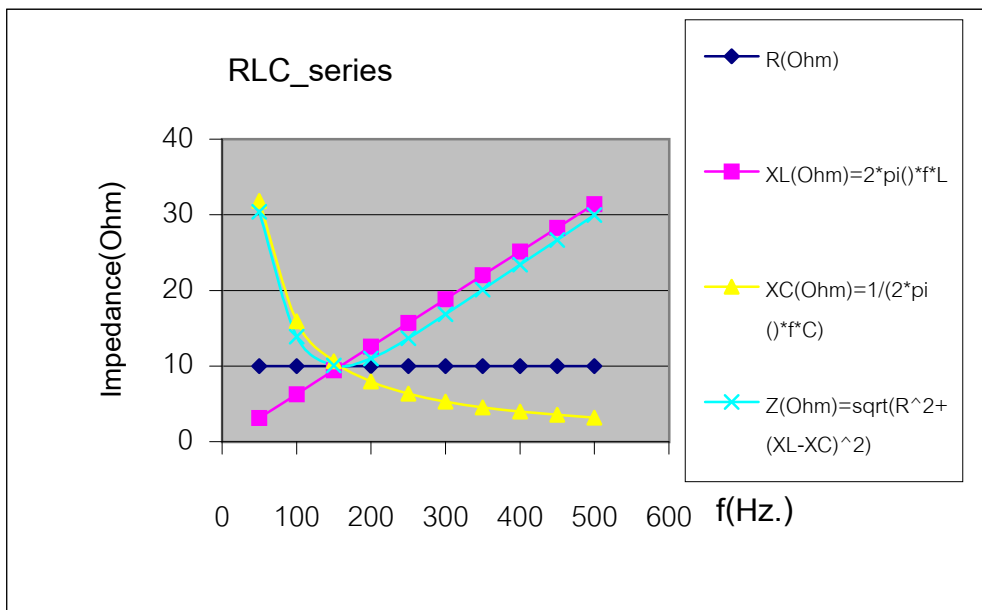


RLC_series; power_factor = $\cos\phi$

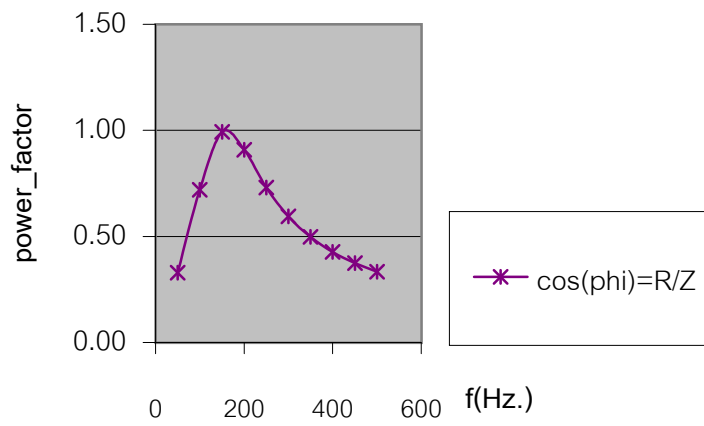


RLC_series; $I_{rms} = V_{rms}/Z$

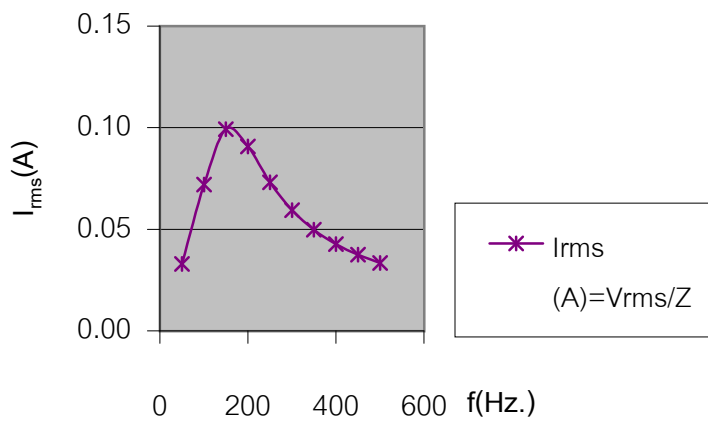

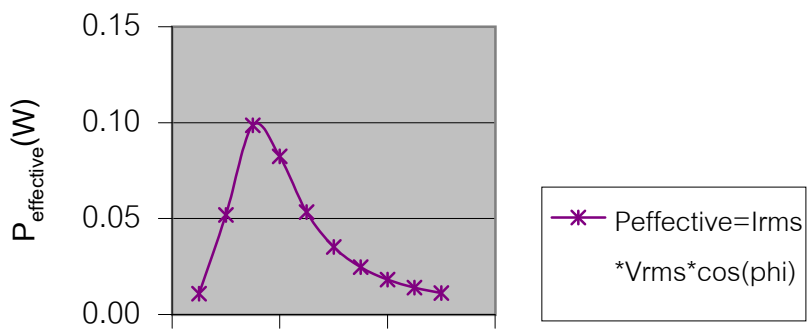RLC_series; $P_{effective} = I_{rms} * V_{rms} * \cos\phi$



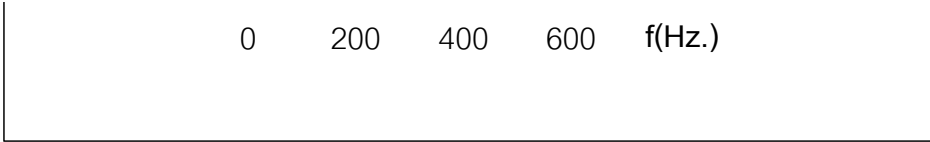

item8 $I=5\sin(1000t)$

$I=I_m\sin(2\pi f t)=\sin(\omega t)$

question1 $P_{avg}(W)=?$

$P_{effective}(W)=I_{rms}\cdot V_{rms}\cdot \cos\phi$

question2 $V_{RL,max}(V)=I_{max}\cdot Z$

no._RL_ser	var	value	EXCEL_COPDE
1	$L(H)=$	0.03	=0.03
2	$R(Ohm)=$	40.00	=40
3	$I_m(A)=$	5.00	=5
4	angular speed(ω ,rad/s)=	1000.00	=1000
5	$f(Hz.)=1000/(2\pi)$	159.15	=\$C\$205/(2*PI())
7	$X_L(Ohm)=2\pi f L$	30.00	=2*PI()*\$C\$206*\$C\$202
8	$Z=\sqrt{R^2+X_L^2}$	50.00	=SQRT(\$C\$203^2+\$C\$207^2)
9	$V_{RL,max}(V)=I_{max}\cdot Z$	250.00	=\$C\$204*\$C\$208
10	power_factor= $\cos\phi=R/Z$	0.80	=\$C\$203/\$C\$208
11	$I_{rms}(A)=I_{max}/\sqrt{2}$	3.54	=\$C\$204/SQRT(2)
12	$V_{rms}(V)=V_{max}/\sqrt{2}$	176.78	=\$C\$209/SQRT(2)
13	$P_{effective}(W)=I_{rms}\cdot V_{rms}\cdot \cos\phi$	500.00	=\$C\$211*\$C\$212*\$C\$210

item9 PH40205,P187

<http://sathaporn.exteen.com/20070517/m6062550g2>

item10 $\text{Vector}_v = \text{Vector}_E \times \text{Vector}_B =$

cross vector product

i	j
Ex	Ey
Bx	By

$\text{Vector}_v = \text{Vector}_E \times \text{Vector}_B =$

i	j	k
0	0	0
-Bx	0	0

$$\text{Vector}_v = \text{Vector}_E \times \text{Vector}_B = +i[(0 \cdot 0 - 0 \cdot E_z)] - j[(0 \cdot 0 - (-B_x)(+E_z)] + k[(0 \cdot 0 - (-B_x)(0)]$$

$$\text{Vector}_v = \text{Vector}_E \times \text{Vector}_B = +i[0] - j[(B_x E_z)] + k[0]$$

$$\text{Vector}_v = \text{Vector}_E \times \text{Vector}_B = -j(B_x E_z)$$

Note

V_L definition

$$d(\cos(\theta))/d(\theta) = -\sin(\theta)$$

$$d(\theta)/dt = \omega$$

$$X_L = \omega L = 2\pi fL$$

Ohm's Law

$$V_{L_o} = X_L \cdot I_o$$

Note

Ohm's Law

$$V_{R_o} = I_o \cdot R$$

Hypothesis

LHS=RHS

Ohm's Law

input $V_{co} =$
1
$V_C = -V_{Co} \cdot \sin(\theta)$
0.00

-0.71
-1.00
-0.71
0.00
0.71
1.00
0.71
0.00
y4

]

SELF_TEST	ans(TRUE=1,FALSE=0)	mark	sum_mark	pass_mark
159.15	TRUE	1	1	4.2
	FALSE	0		
	FALSE	0		
	FALSE	0		

	FALSE	0		
	FALSE	0		

Self_test	check_ANS	mark	sum_mark	summary_pass
30	TRUE	1	1	not_pass
	FALSE	0		
	FALSE	0		
	FALSE	0		
	FALSE	0		
	FALSE	0		
	FALSE	0		

Self_test	check_ANS	mark	sum_mark	sum_mark%
1.00E+07	TRUE	1	1	25%
	FALSE	0		
	FALSE	0		
	FALSE	0		

C(μ F)	fresonace(Hz.)= $1/[2*\pi()*\text{sqrt}(L*C)]$		Vrms(V)	
100	\updownarrow	1.59E+02		1 \updownarrow
$X_C(\text{Ohm})=1/(2*\pi()*f*C)$	$Z(\text{Ohm})=\text{sqrt}(R^2+(X_L-X_C)^2)$	$\cos(\text{phi})=R/Z$	$I_{\text{rms}}(\text{A})=V_{\text{rms}}/Z$	$P_{\text{effective}}=I_{\text{rms}}*V_{\text{rms}}*\cos(\text{phi})$
31.83	30.38	0.33	0.03	0.01
15.92	13.88	0.72	0.07	0.05
10.61	10.07	0.99	0.10	0.10
7.96	11.01	0.91	0.09	0.08
6.37	13.68	0.73	0.07	0.05
5.31	16.84	0.59	0.06	0.04
4.55	20.11	0.50	0.05	0.02
3.98	23.40	0.43	0.04	0.02
3.54	26.68	0.37	0.04	0.01
3.18	29.95	0.33	0.03	0.01
y3	y4	y5	y6	y7

summary
not_pass



